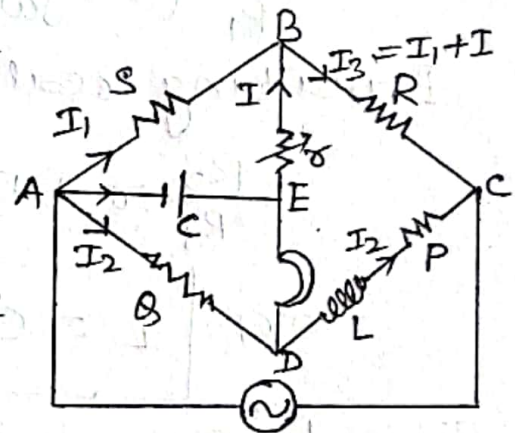


## Value of 'L' using A.C. Bridge

Anderson's Bridge :- This is one of the most common bridges for accurate measurement of inductance. In this method the self inductance is expressed in terms of a standard capacitor.

The connections are shown in figure. At first a battery and a moving coil galvanometer are used to obtain a balance for steady currents by



adjusting the resistance in the four arms of the bridge as usual. Next an A.C. source and a pair of head phones (H.P) are used and the A.C. balance is obtained by adjusting non-inductive resistance  $r$  in series with the capacitor  $C$ .

At the time of balance the potential at E is equal to the potential at D. Applying Kirchhoff's laws we have for mesh ABEA

$$R_1 I_1 - \left( r + \frac{1}{j\omega C} \right) I = 0 \quad \text{--- (1)}$$

for mesh AEDA,

$$I \left( \frac{1}{j\omega C} \right) - R_3 I_2 = 0 \quad \text{--- (2)}$$

and for mesh

$$R_2 (I_1 + I) - (j\omega L + R_4) I_2 + I r = 0 \quad \text{--- (3)}$$

from equation (1)

$$I_1 = \left( \gamma + \frac{1}{j\omega C} \right) \frac{I}{R_1}$$

and from equation (2)

$$I_2 = \left( \frac{1}{j\omega C} \right) \frac{I}{R_3}$$

Substituting these values of  $I_1$  and  $I_2$  in eqn (3) we have,

$$\frac{R_2}{R_1} \left( \gamma + \frac{1}{j\omega C} \right) I + R_2 I - \frac{(j\omega L + R_4)}{j\omega C \cdot R_3} I + I\gamma = 0$$

Equating real and imaginary parts, we get

$$\frac{R_2}{R_1} \gamma + R_2 - \frac{L}{CR_3} + \gamma = 0$$

$$\text{or, } \boxed{L = CR_3 \left[ \gamma \left( 1 + \frac{R_2}{R_1} \right) + R_2 \right]} \quad (4)$$

$$\text{and } \frac{R_2}{R_1 \omega C} - \frac{R_4}{R_3 \omega C} = 0$$

$$\text{or, } \frac{R_2}{R_1} - \frac{R_4}{R_3} = 0$$

$$\text{or, } \frac{R_2}{R_1} = \frac{R_4}{R_3}$$

$$\text{or, } \boxed{\frac{R_1}{R_2} = \frac{R_3}{R_4}} \quad (5)$$

These conditions are independent of frequency of the source and can be satisfied independently of each other by adjusting  $R_4$  in eqn (5) and  $\gamma$  in equation (4). Equation (4) shows that the A.C balance is possible only when  $L > CR_2 R_3$  otherwise  $\gamma$  will be negative. It is best to use  $R_1 : R_2 = 1 : 1$ . Then the above equation reduces to

$$R_3 = R_4 \text{ and } L = CR_3 (2\gamma + R_2) \quad (6)$$